

**THREE YEAR B.Sc. (CBCS) DEGREE EXAMINATIONS :: 2022**  
**SECOND SEMESTER**  
**PART II: ELECTRONICS**  
**DIGITAL ELECTRONICS**  
 (New Regulations : 2020-21)

Time 3 hours

Max. Marks: 75

**SECTION - A**Answer any **THREE** of the following

Each question carries 5 marks

(5 x 5 = 25 marks)

1. Write a brief note on excess-3 code.
2. Write a brief note on BCD code.
3. Briefly mention the laws of Boolean algebra.
4. Discuss 4-input NOR gate.
5. Explain the working of a half-adder.
6. Briefly explain the working of 4:1 multiplexer.
7. Discuss the working of RS flip-flop along with their truth tables.
8. Discuss serial in and serial out registers.
9. Briefly explain EEPROM.
10. Discuss EAROM.

**SECTION - B**Answer **ALL** question

Each question carries 10 marks

(5 x 10 = 50 marks)

11. (a) i. Subtract  $25_{(10)}$  from  $50_{(10)}$  using 1's complement method.  
 ii. Subtract  $20_{(10)}$  from  $15_{(10)}$  using 1's complement method.

**(OR)**

- (b) Explain 9's and 10's complement method of subtraction with suitable examples.

**P.T.O**



12. (a) State and prove Demorgan's theorems.

(OR)

(b) Simplify the Boolean functions,  $F(A, B, C) = \sum m(0, 1, 6, 7) + \sum d(3, 5)$  using a three variable Karnaugh map method and implement the simplified function using NAND gates.

13. (a) Explain the working of Full-adder circuit with the help of truth tables.

(OR)

(b) Discuss the working of 8-line to 3-line encoder.

14. (a) Explain the working of J-K and master-slave flip-flop.

(OR)

(b) Discuss the working of parallel in and parallel out registers.

15. (a) Explain the working of static and dynamic RAM.

(OR)

(b) Discuss the working of PROM and EPROM.

NS2 - 351